 


Hardware Realisierung eines Pipeline A/D-Wandlers

Hardware Realisation of a Pipeline A/D-Converters

Dr. Richard Izak


izak@ieee.org



OTH Regensburg, 20.April 2021

Outline

 - ❑ A/D-Converters: Intro & Architecture differences
- ❑ Cyclic ADC => Pipeline ADC: Increasing the sample rate
- ❑ Circuitry of a Pipeline-ADCs
- ❑ Circuit non-idealities and counter-measures
- ❑ Pipeline-ADC modification and new approaches
- ❑ Outlook and Summary




Basics of Data Conversion

Each digital signal processing system needs a data acquisition channel, an interface to our analog world: ADC and/or DAC

ADC/DAC circuit design is the most challenging field of electronics:

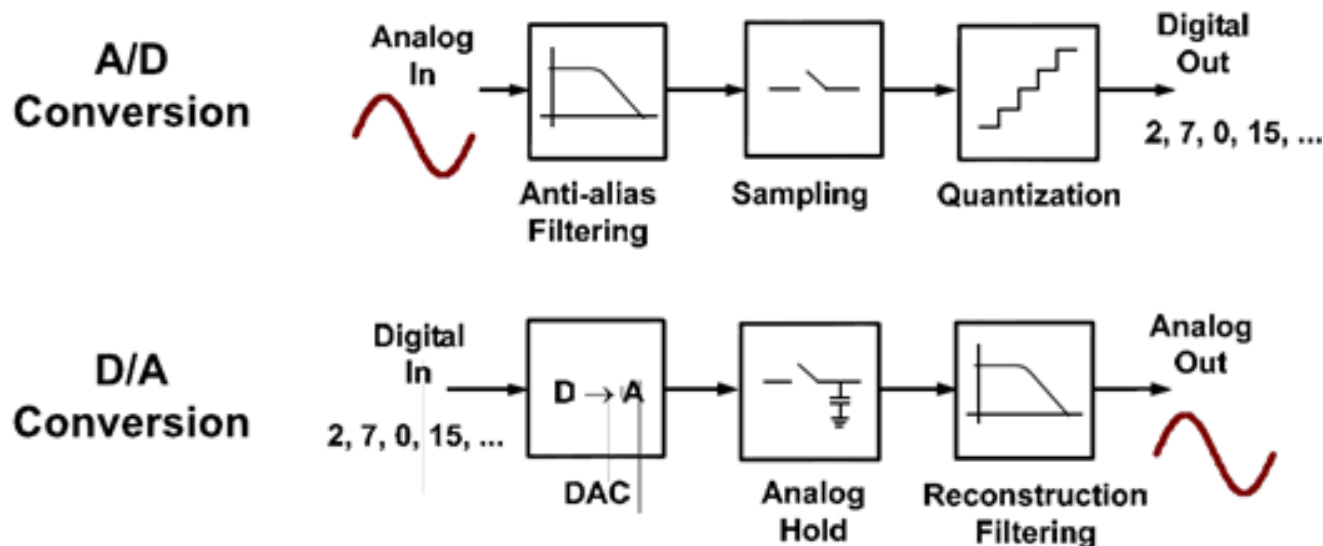- each additional bit of accuracy corresponds to a doubled precision requirements: $10\text{bit} = 2^{-10} = 0,1\% \Rightarrow 20\text{bit} = 2^{-20} = 1\text{ppm}$
- design of data converters needs deep understanding of their spectral properties (system theory)



ADC Architectures

ADC contradiction (design compromise): **Speed** \Leftrightarrow **Accuracy**

- high sample rate (GS/s) with low resolution (6-8-10 bit)

(satCom, early mobCom, digTV)

parallel ADC: Flash, Folding, **(Parallel) Pipeline**, **Bandpass Σ - Δ /CTSD**

- moderate sample (MS/s) rate at moderate resolution (12-14 bit)


Serial ADC / Weighting principles: successive approx. SAR ADC

and cyclic/algorithmic ADC, **Σ - Δ ADC**, **Pipeline ADC**

- low sample rate, very high resolution (20-24 bit)

(process control, precise sensor monitoring, space telescopes)

 - Σ - Δ ADC with high oversampling (OSR)
- integrating & incremental ADC





ADC specification parameters

Static parameters

- ADC offset error, ADC gain error (slope)

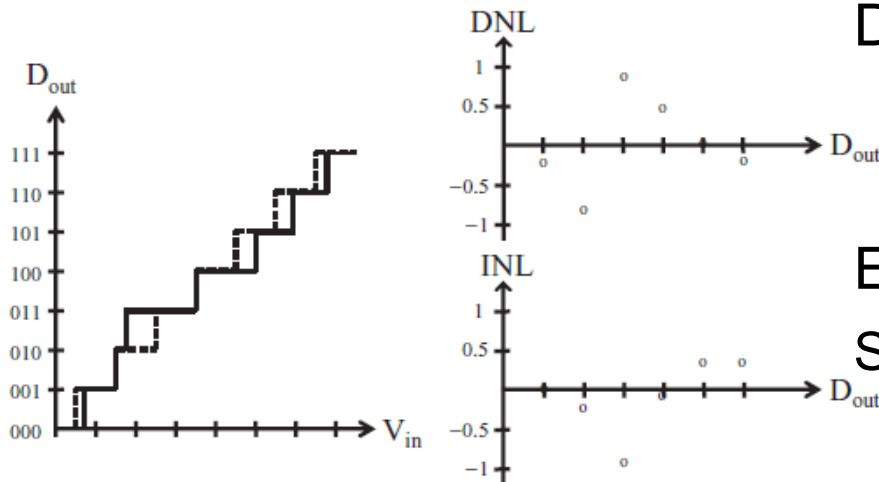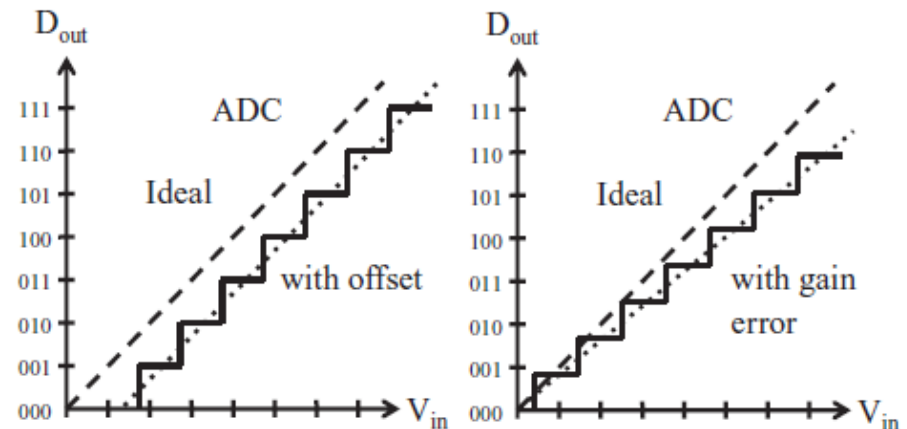- Integral (INL) and Differential (DNL) Non-Linearity



Dynamic performance metrics:
SNR, SNDR, THD, SFDR

in [dB]


ENOB effect. Number of Bits

$$\text{SNDR} = 6,02 \cdot \text{ENOB} + 1,76\text{dB}$$

Serial ADC Architectures


Weighting A/D conversion principle: 1-bit conversion cycle

Successive approximation (SAR)

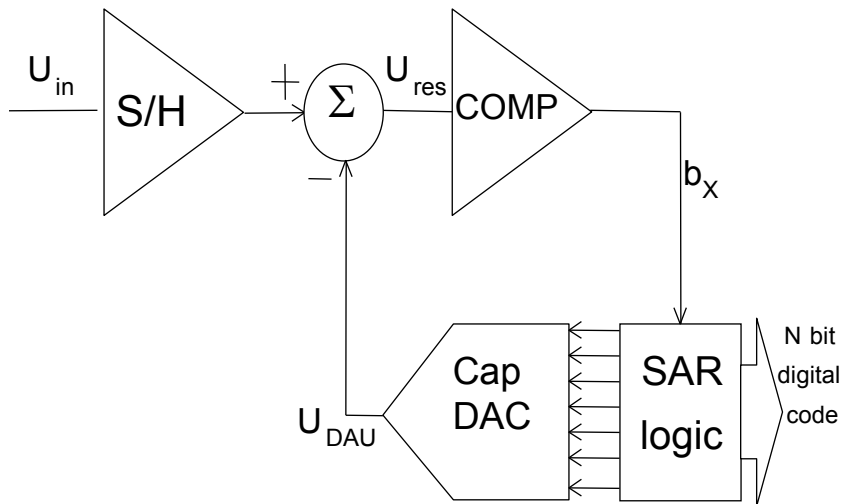

- Simplest circuitry: Comparator, CapArray
- => Higher sampling rate!
- calibration for >11 Bit accuracy required
- large input Cap to be driven (Pre-Amp)
- DAC => key functional block (linearity)


cyclic/algorithmic ADC

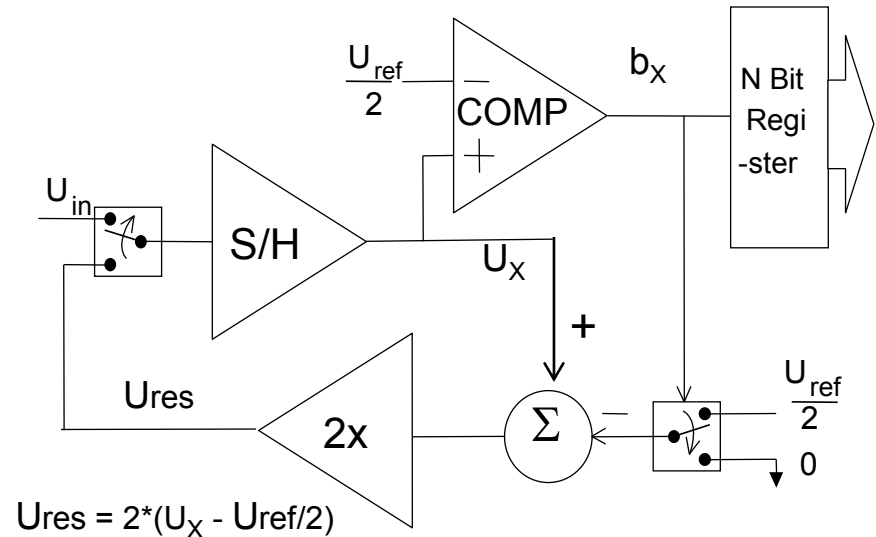


- Full analog circuitry (SC & Amp) => => more R&D complexity
- Offset and Loop-Gain crucial
- Lower area but lower sample rate

Serial ADC: 1b vs. 1.5b cycle

CR: conventional restoring (1b)

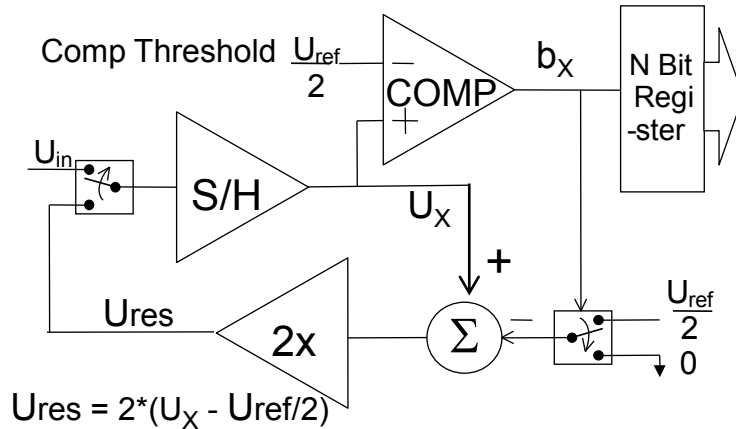


Gray (UC Berkeley) 1984-1990

 


- + Comp offset cancels
- + Loop offset cancels
- + Loop gain relaxed $\frac{1}{2}$

- Reference non-linearity

RSD: redundant signed digit (1.5b)

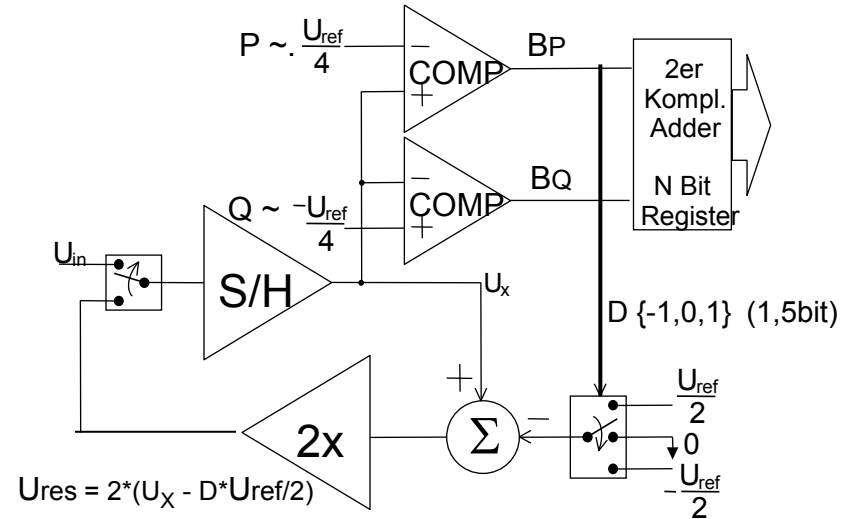


Ginetti SSC'92, Lewis SSC'92

 

Robertson diagram: depiction of the 1b ADC loop transfer function


Serial ADC => parallel ADC

Cyclic ADC: 1b conversion loop

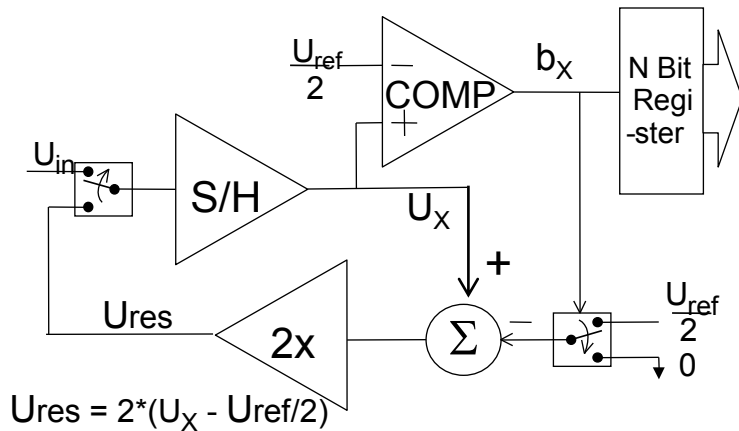

Instead of recycling the ADC loop for conversion for all 12-14 bits => break up the loop and pass the converted residue voltage to the next 1b ADC conversion stage


Pipeline ADC: 1b conversion stage

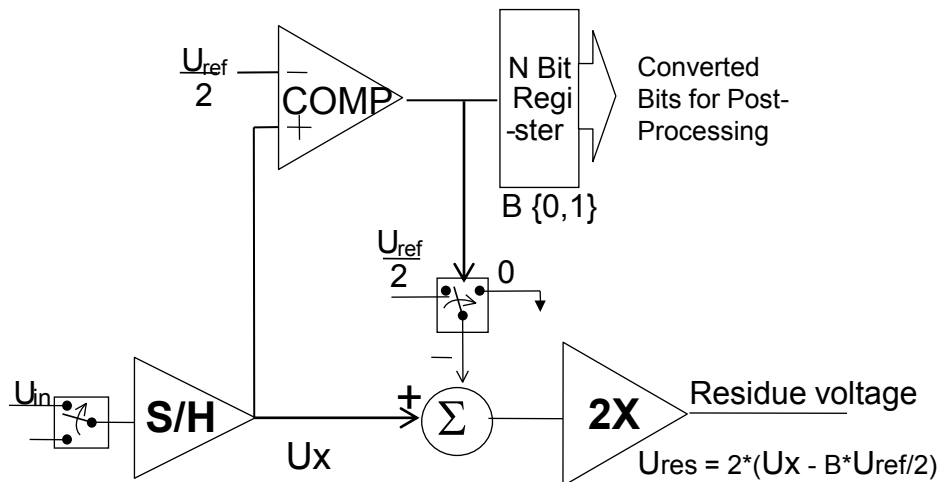

Latency of conversion remains identical, but conversion speed increases! (pipelining principle)

Chip Area and Power Consumption increase (12b pipe => 12x area)

Pipeline ADC

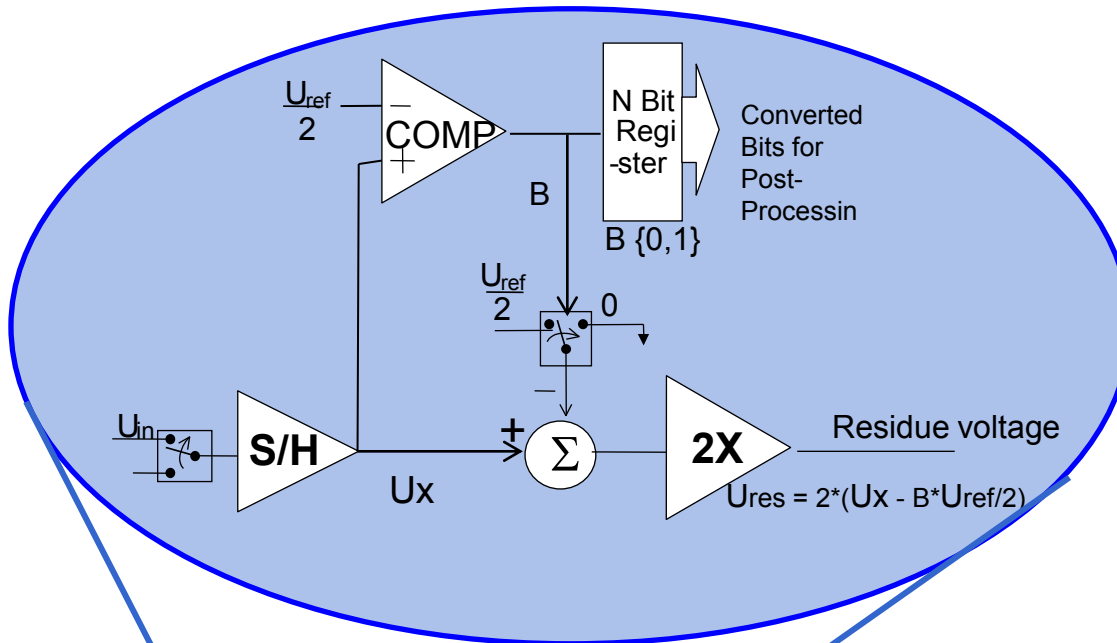


1st stage requires 12b accuracy (SC settling, Amp gain&offset) =>
each following 1b-stages has 1b decreased accuracy requirements
=> speed (shorter cycles) and power scaling (simpler amplifiers)

=> **speed increase by including last stage as 5b flash ADC (no residue)**




Circuit non-idealities

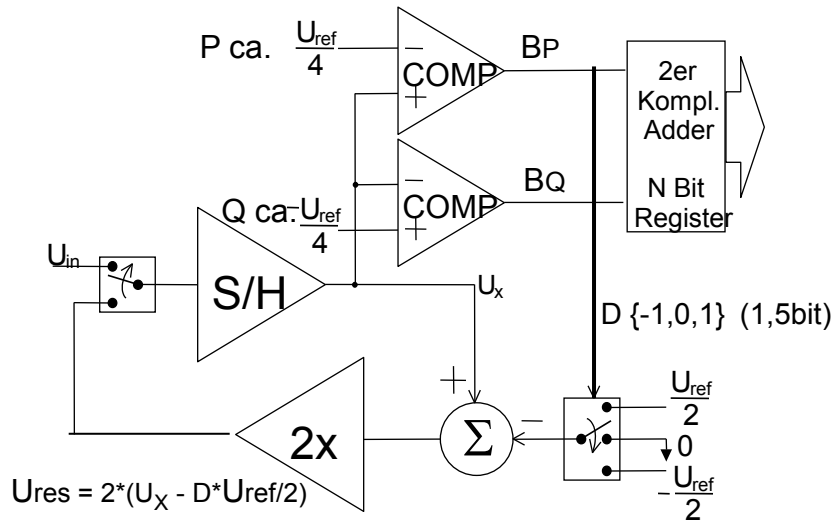

Switched Capacitor (SC) realization of Sample&Hold (S&H) , Reference subtraction and 2x Multiplication/gain

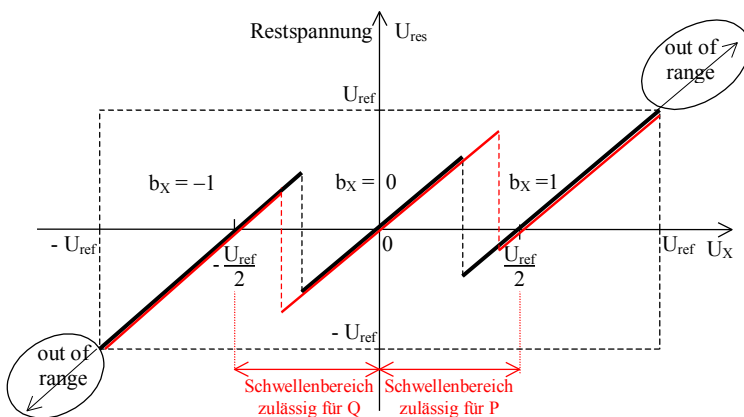Analog circuit realization with operational amplifiers (even if simplest voltage doubling technique by stacking capacitor arose in 2000 Quinn @ Xilinx)



Error sources of analog SC circuitry:

CO = Comparator offset => Missing Codes and Missing Resolution

1.5b RSD conversion cancels this error

lo = Loop offset => Overall Offset + Non-linearity

1.5b RSD conversion cancels this error

ro = Reference offset => Overall Gain error

ge = Loop gain ($\neq 2$) error => Error in linearity (INL,DNL)

Circuit non-idealities

➤ Dynamic Errors

- Sampling- and Jitter-noise (kT/C) => SNR degradation
- additional effects in the near of the frequency-limit caused by the shortened settling process
 - additional OpAmp-, Sampling-, Jitter- noise
 - Frequency limitation of Amplifier (deterioration of ENOB over fin)

Circuit non-idealities

➤ Dynamic Errors

➤ Static Errors (steady state of the settling process)

affecting in the ADC:

- Offset, Overall gain → calibration after A/D conversion possible
- INL, DNL (=> THD) : mainly caused by loop gain-error (x2-operation)


Main physical error-sources and counter-measure solutions :

All effects (except offset) deteriorates the accurate x2-operation

- Capacitors : Capacitor-Mismatch → Ratio independent SC design
- Switches : Clock-Feedthrough → Fully-Differential Technique
- Charge-Injection → Bottom-Plate-Sampling
- OpAmp: Offset & Finite Gain → CDS Techniques | High Gain
- Parasitic Caps: → stray insensitive design, post-layout analysis → layout

SC error compensation

 CDS: correlated double sampling (additional SC phase with dummy Caps) => voltage correction



Prediction phase (error measure):

Transfer operation with Dummy-C's for error estimation

$$C_{e1} = C_{e2}$$

$$\rightarrow U_{C_{e1}} = U_{C_{e2}} = \frac{1}{2} U_{e1}$$


$$C_{x_d} / C_{y_d} = C_x / C_y$$

$$\rightarrow U_{out_d} \approx U_{out}$$

$$\rightarrow U_{e1} \approx U_{e2}$$

but because of charge needed by C_e:
 
$$U_{e2} = (1 + \varepsilon) U_{e1}; \quad \varepsilon \approx (1/G_0) * (C_e / C_y)$$



Operation phase (error compensation):

final Transfer operation with error cancellation

$$U_{e2} - (2 * \frac{1}{2} U_{e1}) \approx 0$$


→ new virtual ground nodes with zero-difference

→ full charge transfer from C_x to C_y

Exact Size of C_e doesn't matter, because of voltage addition

SC error compensation

 CDS: correlated double sampling => charge correction



Prediction phase:

Transfer operation with Dummy-C's for error estimation

$$C_e = C_{e1} = C_{e2} = C_x + C_y \approx 2 * C_x \text{ with } C_x \approx C_y$$


$$\rightarrow Q_{Ce} = U_{e1} * (C_{e1} + C_{e2}) \approx 4 * C_x * U_{e1}$$

$$C_{xD} / C_{yD} = C_x / C_y$$

$$\rightarrow U_{outD} \approx U_{out} \rightarrow U_{e1} \approx U_{e2}$$

but because of charge needed by Ce:
 
$$U_{e2} = (1 + \varepsilon) * U_{e1}; \quad \varepsilon \approx 2 / G_0$$



Operation phase :

final Transfer operation with error compensation

Charge in Ce will be reduced by Qk

$$Q_k = 2 * C_e * (U_{e1} - \frac{1}{2} * U_{e2}) \approx C_e * U_{e2}$$

Error at output is (see before !):

$$U_{out} = U_{e2} * (1 + C_x / C_y) \approx 2 * U_{e2}$$

\rightarrow needed compensation charge is $U_{out} * C_y$



$$\rightarrow Q_k' = U_{e2} * (C_x + C_y) \approx 2 * C_y * U_{e2}$$

\rightarrow Correction is done if $Q_k' = Q_k$: $C_e = C_x + C_y \approx 2 * C_y$

considering charge consumption of Ce (if $C_x = C_y$):


$$\text{exactly: } C_e = 2 * C_x * (1 + \varepsilon) / (1 - \varepsilon)$$

SC error compensation

 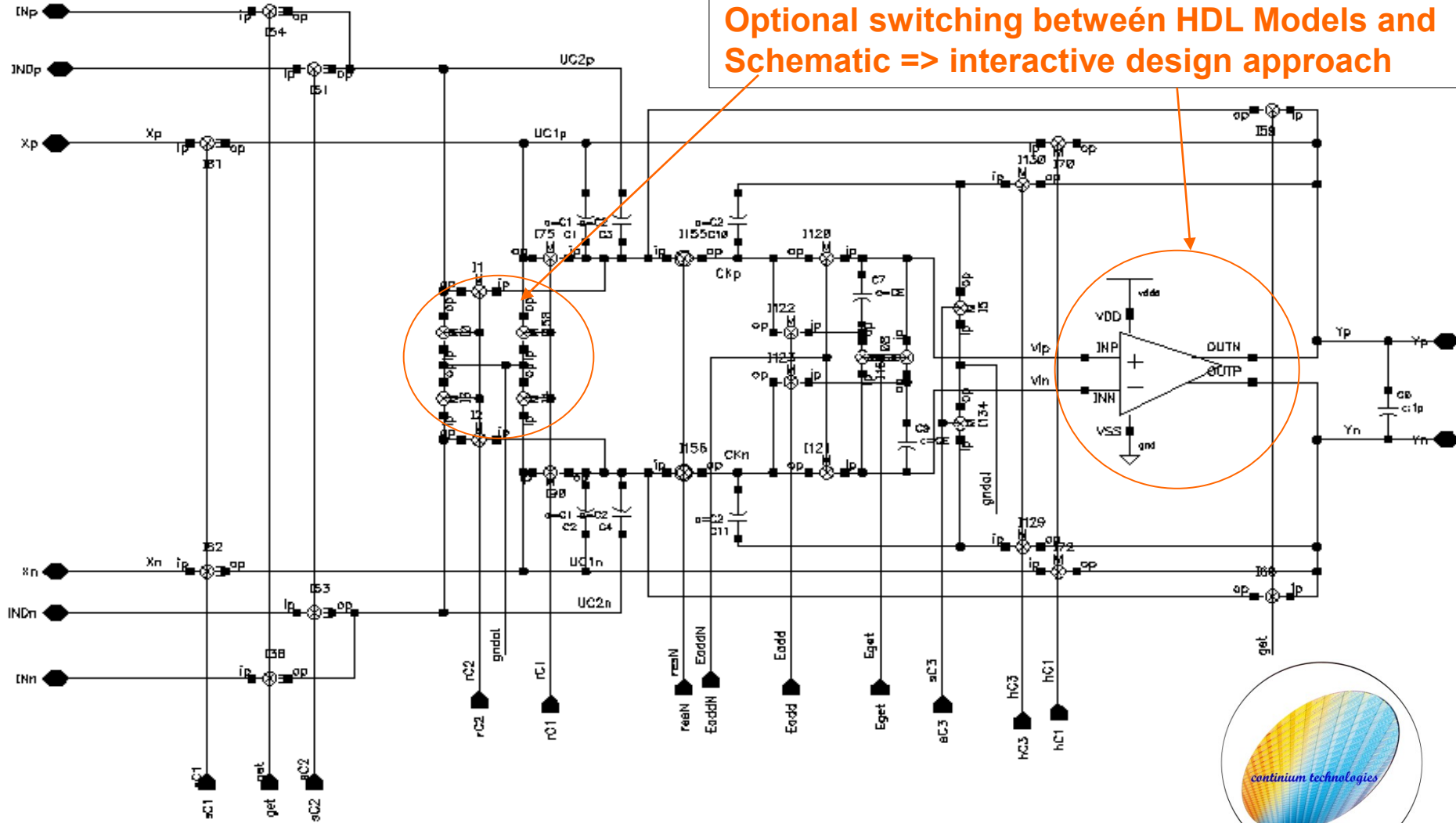


Block level circuit design

Clocked comparator (SC)

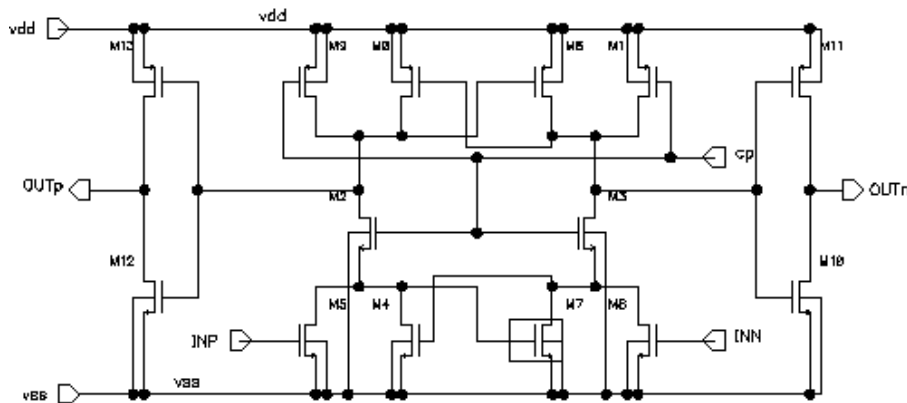

Amp spec	ADC1 (2 stages)	ADC2 (1 stage)
Diff. Gain	101.3 dB	85.5 dB
Unity gain freq. (@ 2pF load)	68.5 MHz	34 MHz
Phase margin (@ 2pF load)	55.7°	71°
Power consumpt.	28 mW	4.3 mW
Chip area	1.5 mm ²	0.11mm ²
Internal compensat.	1.5pF	--

0.6um CMOS in 1999

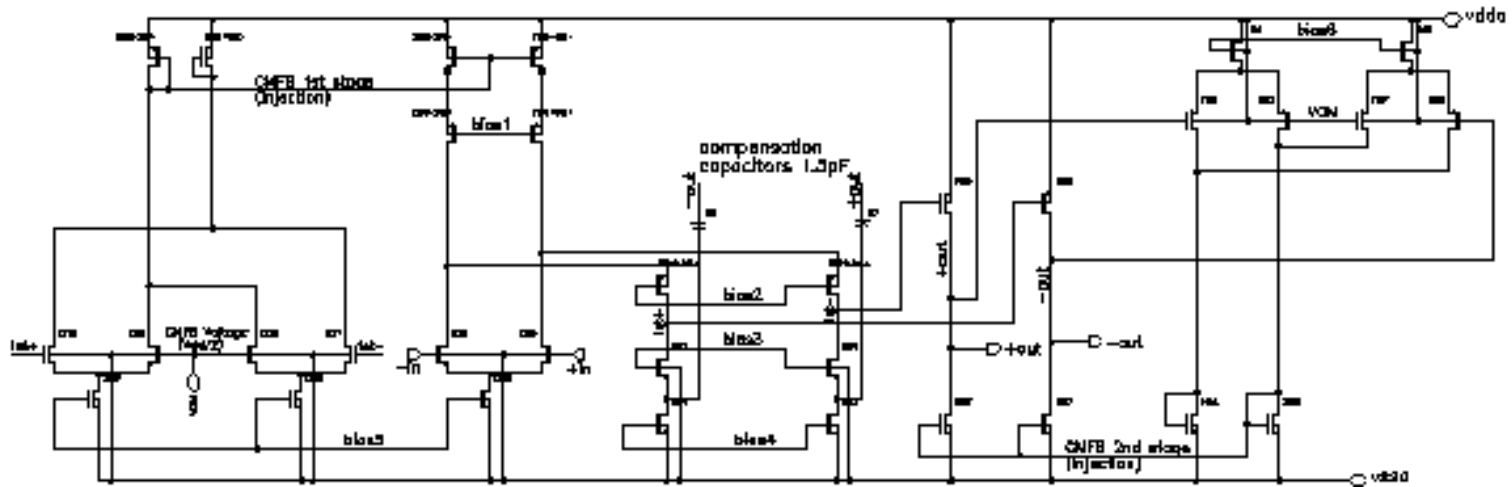




Recent innovation in pipeline ADC

Time-interleaving (parallel pipeline)

Highest speed boost of ADC in recent years:
Ahmed Ali (ADI) 14b 5GS/s in 28nm CMOS

But new challenges arose: digital calibration of
inter-channel offset, gain, clock skew, BW
mismatch!

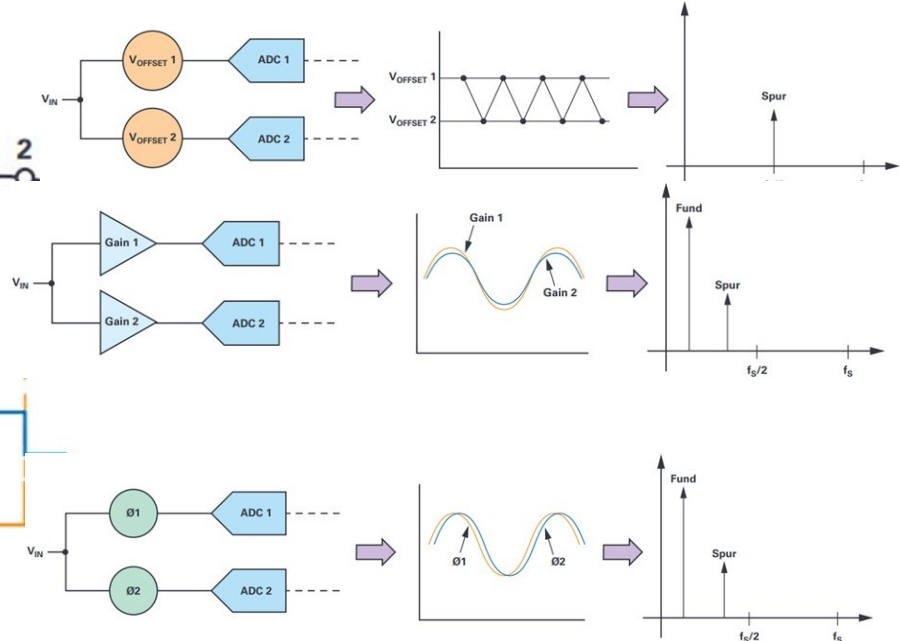 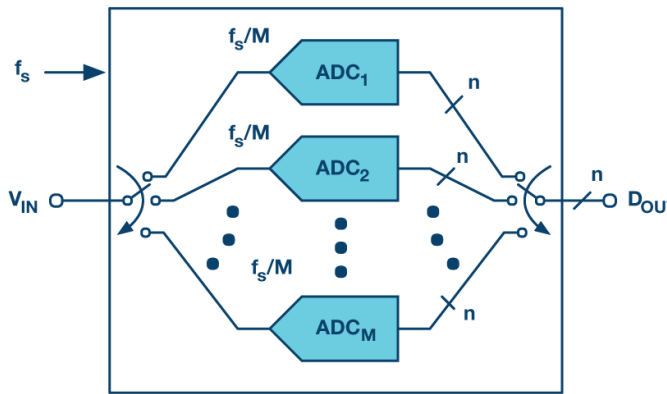
Huge digital post-processing, possible only
thanks to 12-20nm technology progress!



Recent innovation in pipeline ADC

Continuous-Time pipeline ADC

Inherent Anti-Aliasing: DT & CT ADC

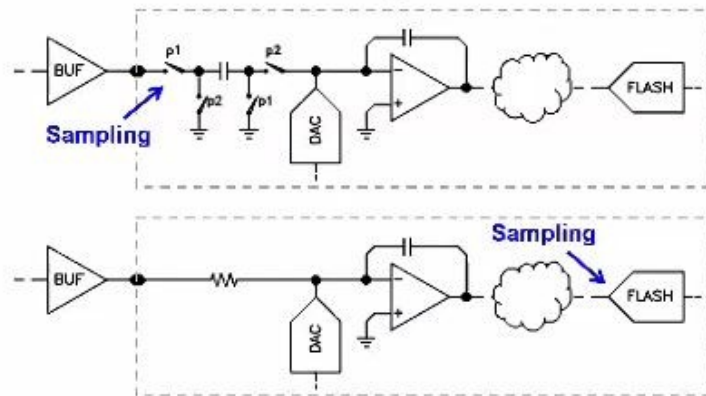


CT offers inherent anti-aliasing
→ Anti-aliasing filter can be relaxed or removed

Combining the advantages from both worlds:

- SC pipeline ADC with large bandwidth
- inherent AA Filter & silent input of CTSD ADC

 5-Stage CT Pipelined ADC in 28nm CMOS [2]



Gubbins/Moon: 2008-2010 publication

Shibata (ADI) 2019-2020 publications

Summary

- ❑ Pipeline ADC architecture derived
- ❑ Non-idealities at system and circuit level discussed
- ❑ Circuit blocks and design solution revealed
- ❑ Further innovation for future pipeline ADCs shown

